

# Cryogenic Adiabatic Transistor Circuits (CATCs)

Erik P. DeBenedictis

Derived from JJ Workshop presentation  
October 21, 2019

# Overview

- Thanks to Mike Frank for inventing 2LAL circa 2000
- Quantum computer scale up creates a new demand for cold, scalable electronics
- Driver: Cryo adiabatic transistor circuits
  - Eject waste energy to room temperature electrically
- Applies to quantum computer control
  - Provides a memory to complement JJs
  - Narrow applicability; won't apply to Exascale
  - Applies to transmons, quantum dot, ion traps
  - Should work at 4 K today; will it work at mK?

# Competitive research

- Paper (TAS early access)

Design and demonstration of an adiabatic-quantum-flux-parametron field-programmable gate array using Josephson-CMOS hybrid memories

Yukihiro Okuma, Naoki Takeuchi, Yuki Yamanashi, *Member, IEEE* and Nobuyuki Yoshikawa, *Senior Member, IEEE*

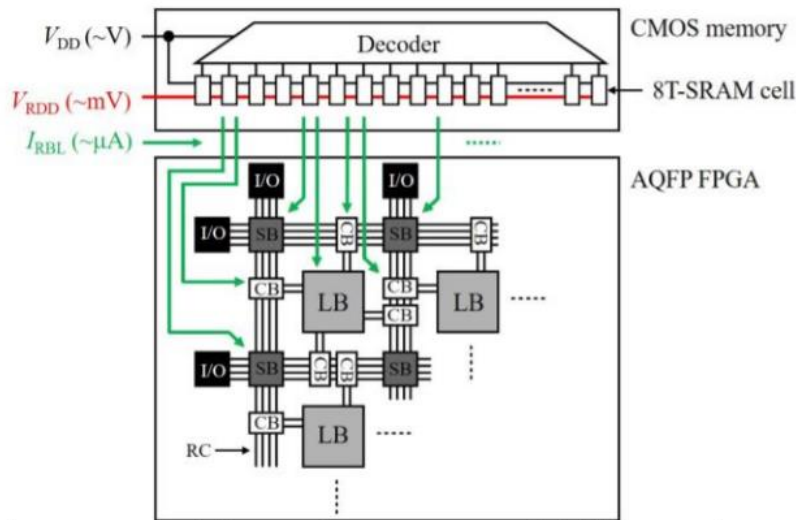


Fig. 1 Conceptual diagram of an AQFP-CMOS hybrid FPGA using a Josephson-CMOS hybrid memory.

- This approach 30,000× more efficient for trans

TABLE II


Junction number, circuit area, memory cell number, power consumption of AQFP-CMOS hybrid FPGAs with two-by-two and 32-by-32 logic cells.

	2×2 logic cell system	32×32 logic cell system
Junction number of AQFP FPGA circuits	1680	313220
Area of AQFP FPGA circuits [μm <sup>2</sup> ]	1960×3350	36085×44600
Number of CMOS memory cells	68	12548
Power consumption of AQFP FPGA circuits [nW]	12.4	2348
Power consumption of CMOS memories [μW]	1.02	188

	JJ	Transistor
Devices	313,220	75,288
Power	2.35E-06	1.88E-04
Power/Dev	7.50E-12	2.50E-09
Power Ratio	1.00	333.11
CATC-JJ	100	1
Advantage	33,311	

# Scalable $(f_{300} \circ f_4 \circ f_{0.015} \circ q)(N)$

<u>Temp</u>	<u>Logic options</u>	<u>Memory-like options</u>
300 K	CMOS	SRAM DRAM Flash
4 K $1,000\times$ overhead	Cryo CMOS JJ SFQ Adiabatic transistor circuit	Excellent progress Adiabatic transistor circuit
15 mK $10^6$ - $10^9\times$ overhead	JJ SFQ Passives Adiabatic transistor circuit ??	Adiabatic transistor circuit ??



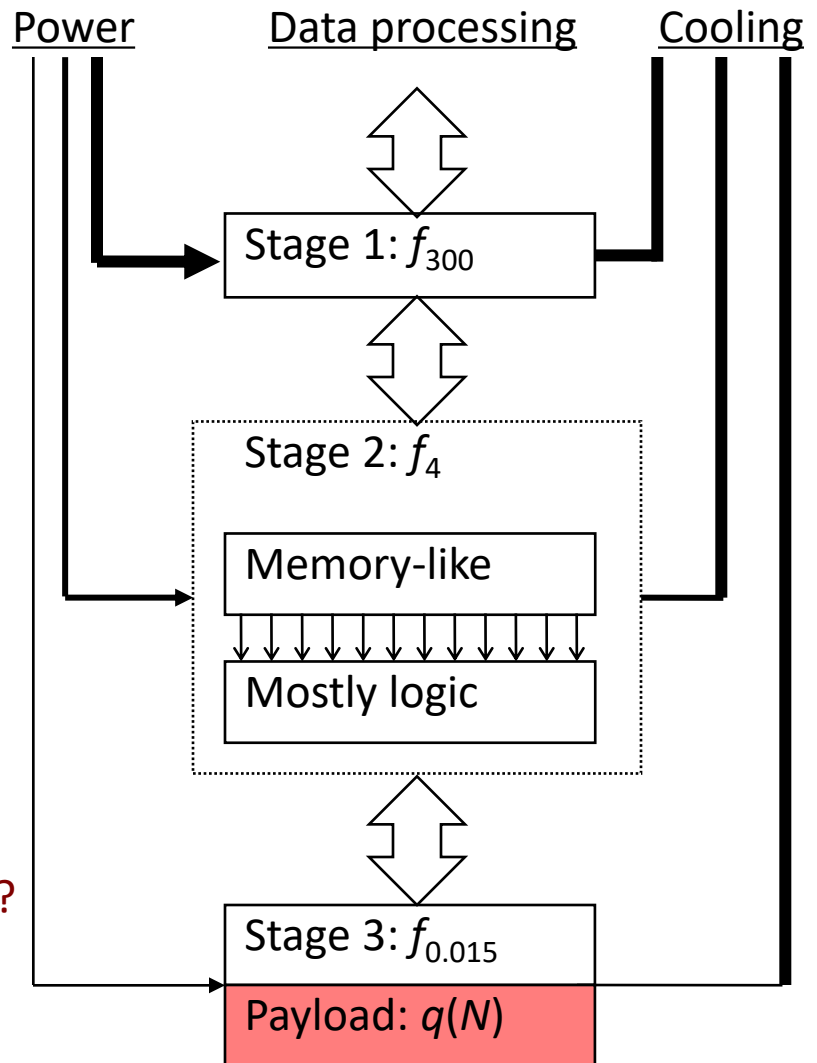


# Cryo CMOS vs. CATC I


- All transistor circuits have  $\frac{1}{2}CV^2$  signal energy
- Adiabatic 2LAL dissipates less in the chip
- How is that possible given conservation of energy?

Energy/op vs. freq., TSMC 0.18, CMOS vs. 2LAL

  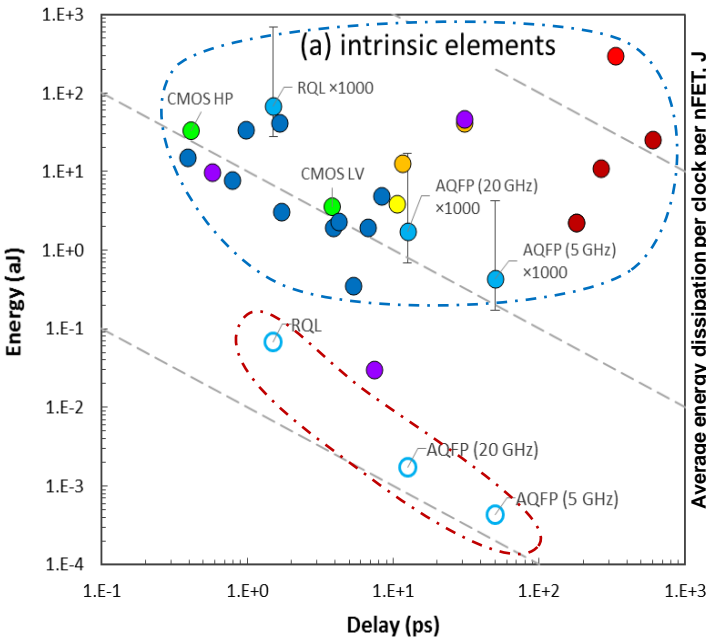Power/device vs. freq., TSMC 0.18, CMOS vs. 2LAL



# Cryo CMOS vs. CATC II

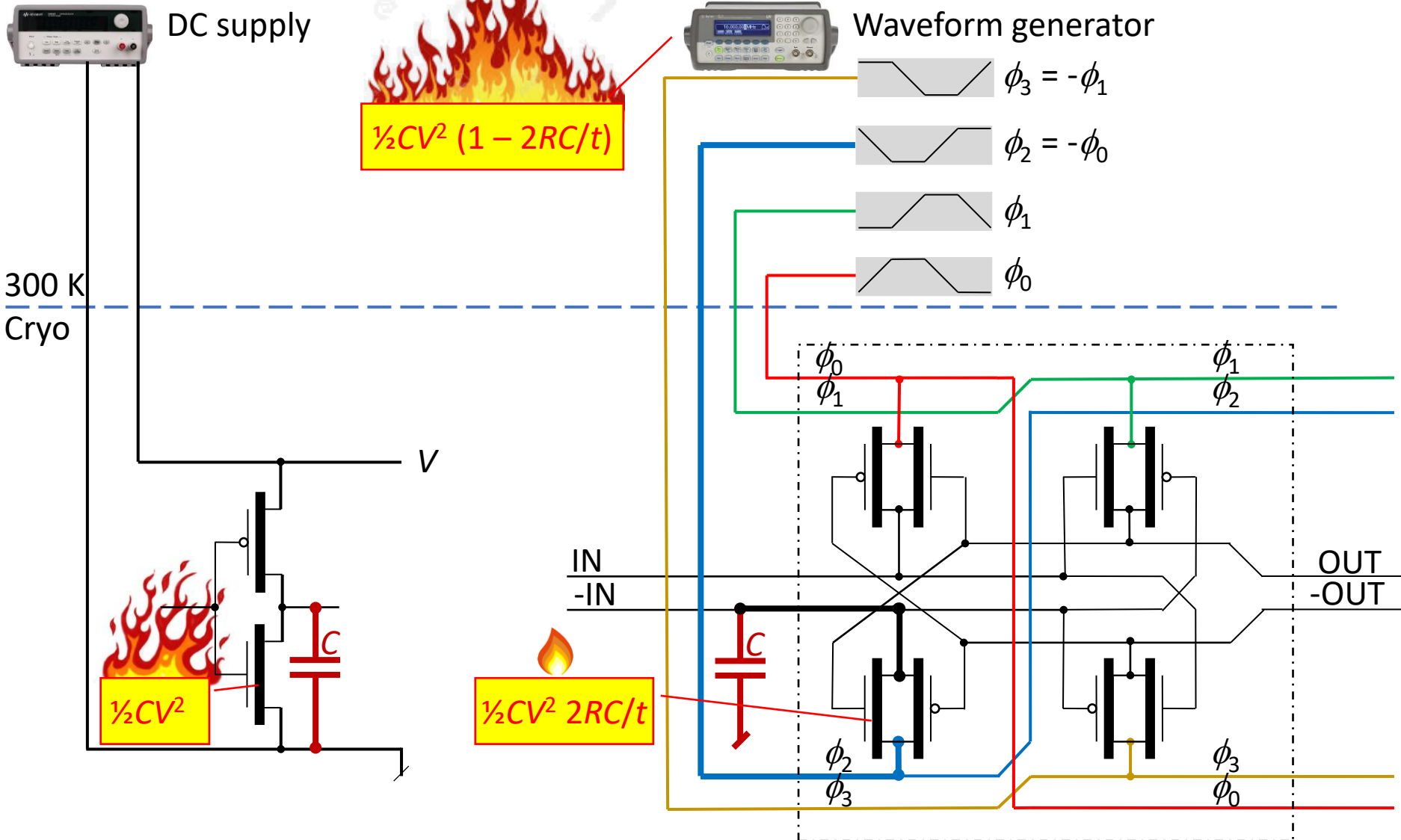

# Backup: Transistor changes

- Transistors used to experience carrier freeze out and 'kinks,' but these effects are no longer a problem due to the natural evolution of transistors
- Some DRAMs and some FPGAs work at 4 K now
  - See for example, FPGA Design Techniques for Stable Cryogenic Operation, arXiv:1709.04190
- This validates that cryo CMOS can work at 4 K
  - Except for imposing a refrigeration load
- New transistor lines for IoT are on the right path
  - Intel 22FFL, GF 22FDX, TSMC 22ULP, or ST 28 FDSOI


# Backup: Basic physics of cooling

- Electric energy is happy to flow through a wire that crosses a temperature gradient in either direction
- Heat flows to a lower temperature unassisted, but needs energy to move to a higher temperature
- Reversible and adiabatic computing tried to recycle energy within a single-temperature system, but the necessary energy-recycling power supply has not been found after decades of looking
- Cryogenic adiabatic transistor circuits move waste across the temperature gradient as energy before turning it into heat, not after


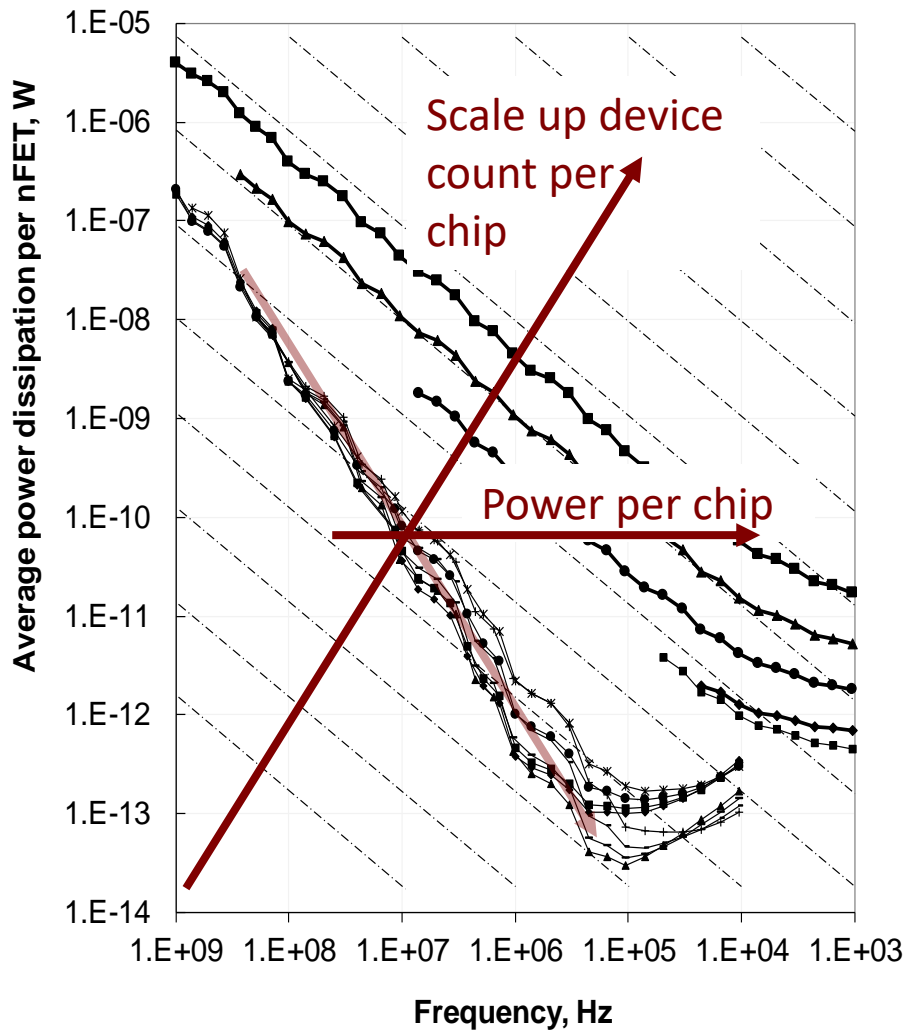
# Adiabatic scaling

Power/device vs. freq., TSMC 0.18, CMOS vs. 2LAL




- Scale up clock period – i. e. slow the clock
- Per-gate dissipation drops quadratically
- But add quadratically more devices at same total power
- No free lunch
  - Supply current rises
  - Transistor leakage
  - Run out of chip space

# Question of the hour

- Can cryogenic adiabatic transistor circuits become the memory counterpart for JJ/SFQ?
- If we follow adiabatic scaling, will ...
  - device count rise enough to comprise a “memory”
  - before speed makes it unusably slow?


# Hybrid technology model

Baseline

 

1,000 cryo CMOS gates (to scale)  
4 GHz clk, 160  $\mu$ W at 4 K

Scaling step 3

 

100 million 2LAL gates (to scale)  
4 MHz clk, 160  $\mu$ W + 167  $\mu$ W (leakage) at 4 K

# Backup: JJ-2LAL scaling steps I

- Each step: 100× gates; 1/10 clock rate; same chip power; static leakage rises with device count
- First step CMOS → 2LAL 10× device penalty

Baseline	$N_{\text{RQL}} = 1 \text{ M}$	$f_{\text{RQL}} = 1.6 \text{ GHz}$	$P_{\text{RQL}} = 160 \text{ } \mu\text{W}$	$P_{\text{Static}} = \text{n/a}$
----------	--------------------------------	------------------------------------	---	----------------------------------

	$N_{\text{CMOS}} = 1 \text{ K}$	$f_{\text{CMOS}} = 4 \text{ GHz}$	$P_{\text{CMOS}} = 160 \text{ } \mu\text{W}$	$P_{\text{Static}} = \text{n/a}$
--	---------------------------------	-----------------------------------	--	----------------------------------

Scaling Step 1	$N_{\text{RQL}} = 1 \text{ M}$	$f_{\text{RQL}} = 1.6 \text{ GHz}$	$P_{\text{RQL}} = 160 \text{ } \mu\text{W}$	$P_{\text{Static}} = \text{n/a}$
----------------	--------------------------------	------------------------------------	---	----------------------------------

	$N_{\text{2LAL}}^{(1)} = 10 \text{ K}$	$f_{\text{2LAL}}^{(1)} = 400 \text{ MHz}$	$P_{\text{2LAL}}^{(1)} = 160 \text{ } \mu\text{W}$	$P_{\text{Static}}^{(1)} = 16.7 \text{ nW}$
--	--	---	--	---

Scaling Step 2	$N_{\text{RQL}} = 1 \text{ M}$	$f_{\text{RQL}} = 1.6 \text{ GHz}$	$P_{\text{RQL}} = 160 \text{ } \mu\text{W}$	$P_{\text{Static}} = \text{n/a}$
----------------	--------------------------------	------------------------------------	---	----------------------------------

	$N_{\text{2LAL}}^{(2)} = 1 \text{ M}$	$f_{\text{2LAL}}^{(2)} = 40 \text{ MHz}$	$P_{\text{2LAL}}^{(2)} = 160 \text{ } \mu\text{W}$	$P_{\text{Static}}^{(2)} = 1.67 \text{ } \mu\text{W}$
--	---------------------------------------	--	--	---

Scaling Step 3	$N_{\text{RQL}} = 1 \text{ M}$	$f_{\text{RQL}} = 1.6 \text{ GHz}$	$P_{\text{RQL}} = 160 \text{ } \mu\text{W}$	$P_{\text{Static}} = \text{n/a}$
----------------	--------------------------------	------------------------------------	---	----------------------------------

	$N_{\text{2LAL}}^{(3)} = 100 \text{ M}$	$f_{\text{2LAL}}^{(3)} = 4 \text{ MHz}$	$P_{\text{2LAL}}^{(3)} = 160 \text{ } \mu\text{W}$	$P_{\text{Static}}^{(3)} = 167 \text{ } \mu\text{W}$
--	---	---	--	--

# Backup: JJ-2LAL scaling steps II

- Each step: 100× gates; 1/10 clock rate; same chip power; static leakage rises with device count
- First step CMOS → 2LAL 10× device penalty

Baseline	$N_{\text{RQL}} = 1 \text{ M}$	$f_{\text{RQL}} = 1.6 \text{ GHz}$	$P_{\text{RQL}} = 160 \mu\text{W}$	$P_{\text{Static}} = \text{n/a}$
	$N_{\text{CMOS}} = 1 \text{ K}$	$f_{\text{CMOS}} = 4 \text{ GHz}$	$P_{\text{CMOS}} = 160 \mu\text{W}$	$P_{\text{Static}} = \text{n/a}$
	Device count rises $10^5$	Speed drops 1,000×	Chip is now full; power rises 3×	
Scaling Step 3	$N_{\text{RQL}} = 1 \text{ M}$	$f_{\text{RQL}} = 1.6 \text{ GHz}$	$P_{\text{RQL}} = 160 \mu\text{W}$	$P_{\text{Static}} = \text{n/a}$
	$N_{\text{2LAL}}^{(3)} = 100 \text{ M}$	$f_{\text{2LAL}}^{(3)} = 4 \text{ MHz}$	$P_{\text{2LAL}}^{(3)} = 160 \mu\text{W}$	$P_{\text{Static}}^{(3)} = 167 \mu\text{W}$

# JJ $\mu$ wave Components


$\mu$ wave SPST  
switch



- There is a need to control microwaves at cryo
  - Northrop-Grumman, Google (Naaman)
  - Transmon quantum computers, etc.
- However, all current options require control signals from room temperature, limiting scalability
 
# JJ FPGAs proposed


Reconfigurable  
Josephson  
junction (FPGA)



- Refs.: Fourie and Katam
- However, the configuration logic is via JJs, so the result is not very dense

 
# Hybrid 2LAL-JJ controller

Reconfigurable  
Josephson  
junction (FPGA)





Controlled  
layer

Configuration  
layer

 


Adiabatic shift  
register  
memory

  



# Quantum program with FPGA overlays

Reconfigurable Josephson junction (FPGA)

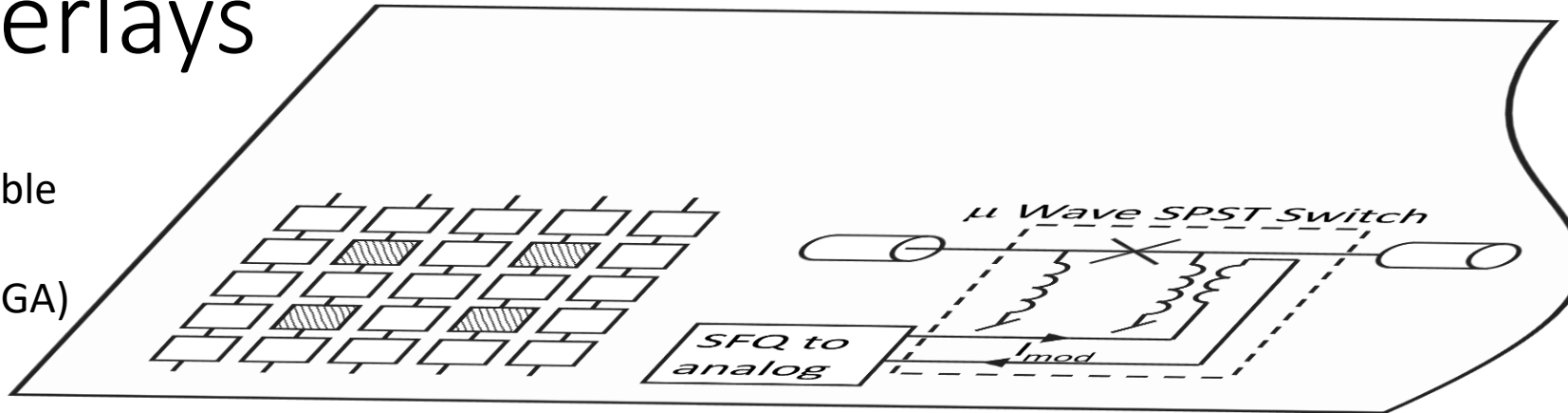

Program via FPGA overlay

Self test
Qubit initialization
Quantum program
Qubit readout

- Reconfiguration time estimate 250 ns
- Qubit decoherence time 10s of  $\mu$ s
- Qubit state can persist across a reconfiguration

# Conclusions

- Paper <http://www.zettaflops.org/CATC>
- Pre quantum supremacy brings attention to scalable control systems for quantum computes
- Cryogenic adiabatic transistor circuits are helpful due to a principle related to temperature
  - “dissipate the heat at 300 K”
- System designers expect a suite of technologies
  - Smartphones need CMOS + DRAM + Flash
  - Cryo systems need JJs + Cryo adiabatic transistor circuits
- Further work:
  - Test hybrid of JJ + 22FFL, 22FDX, 22ULP, or ST 28 FDSOI
  - Test architectures applicable to quantum computer control
  - Rebalance transistors

# IEEE Transactions on Quantum Engineering

**Status:** Proposed for approval November 2019, first issue January 2020

**Call to action:** Precollecting manuscripts now for peer review.

If interested, talk to anybody on this slide.

**Open access charge subsidized for manuscripts submitted by December 31, 2019 (IEEE CSC)**

**Pub. model:** Continuously published [Gold Open Access](#),  
format same as “IEEE Access”

**Erik DeBenedictis**, proposed and acting EIC, **Oleg Mukhanov**, assoc. editor, **Britton Plourde**, reviewer, **Adriana E. Lita** and **Ryan Camacho**, photonics. *Seeking additional associate editors*

**Sponsors:** IEEE CSC, Magnetics, Microwave, Photonics, and Signal Proc. Societies

**Scope:** TQE covers quantum engineering within IEEE’s scope of electrical and electronic engineering.



Backup

# Backup: Transistor properties

- Based on Spice simulations, 4 K quantum computer controllers need to scale 50-72 qubits to the next step should work with Intel 22FFL, GF 22FDX, TSMC 22ULP, ST 28 FDSOI “out of box”
- Custom transistors would help, may not be that different
  - Need ultra-low leakage, i. e. high  $I_{on}/I_{off}$  ratio
  - Quantum computer performance comes from the qubits, so the traditional CMOS metrics don't hold
  - Natural steepening of subthreshold slope give maneuvering room; need thicker oxide and threshold adjustment at some point

# Backup: Architectural issues

(Cryogenic Adiabatic Transistor Circuit = CATC)

- The CATC advantage is narrow
  - CATCs are slow; need to be a hybrid with something fast to be useful. Fortunately, a CATC-JJ hybrid is natural
  - Memory needs to be dense. Fortunately, CATCs are nearly as dense as transistors, far denser than JJs
  - CATCs are not fast enough to be the addressing logic for RAM, but CATCs work for memory-like structures like shift registers
- FPGAs and buffers
  - Quantum computer controllers are halfway between signal processors and general purpose computers

# Backup Cold, scalable controller

- Hybrid FPGA
  - Configured logic: JJs, configuration logic: transistors
  - Problem: JJs are huge
  - Solution: FPGA “timeshares” JJs by on-the-fly reconfiguration
- All-cold SFQ microwave components
  - There is a suite of switches, modulators, etc. available, but they require waveforms piped in from 300 K
  - While we don't know how to make a random access cryo memory, waveforms are accessed as a stream, making the shift register in previous slides sufficient