

# Cryogenic Adiabatic Transistor Circuits (CATC) for Quantum Computer Control

Workshop on Low Temperature Electronics WOLTE 14,  
April 14, 2021


Erik P. DeBenedictis  
Zettaflops, LLC

# Summary

- Enabling idea:
  - CMOS means (1) transistors and (2) a circuit
  - Let us use the same transistors in a different circuit
- Benefits:
  - $\sim 1/1,000$  energy or heat in the cryostat
  - Lower noise in terms of power/amplitude
  - Noise can be below qubit control at frequencies
  - Example cryo FPGA hybrid (e. g. reconfigurable logic)
- See <https://zettaflops.org/q2lal>
  - Preprint of extended abstract; Q2LAL circuit paper


# Use Case: Classical Control of Quantum Computers

- Some classical function should be near qubits
  - Set to  $|0\rangle$  by measure and conditional NOT
  - Quantum error correction
  - Magic state factories
- Example from talk
  - Magic state factory

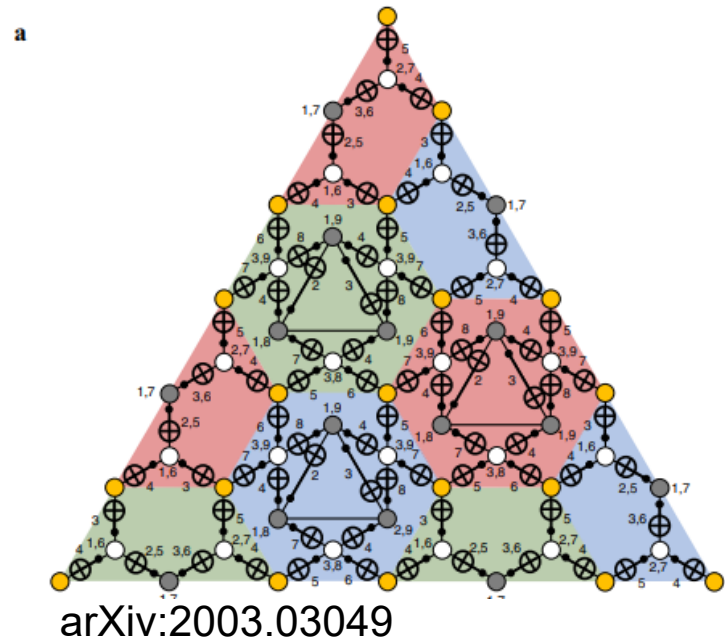
 
# Adiabatic Circuits

- Energy/op vs. clock period
- CMOS constant energy/op
- Adiabatic energy per op drops with clock period
- 1000× energy efficiency increase reasonable




# Quiet 2 Level Adiabatic Logic

## Q2LAL power-clocks


- Ramped power-clocks charge transistors gates
- No abrupt charging

①

 

 
## Q2LAL power train

- Power-clocks charge transistor gates) and then leave by reflection




# Even-load Adiabatic Logic Family Based on Cyber Security


(a) Circuit reference

 

(b) S2LAL signaling

 


(d) Q2LAL signaling

 


(c) S2LAL + inverter

Cumulative dissipation

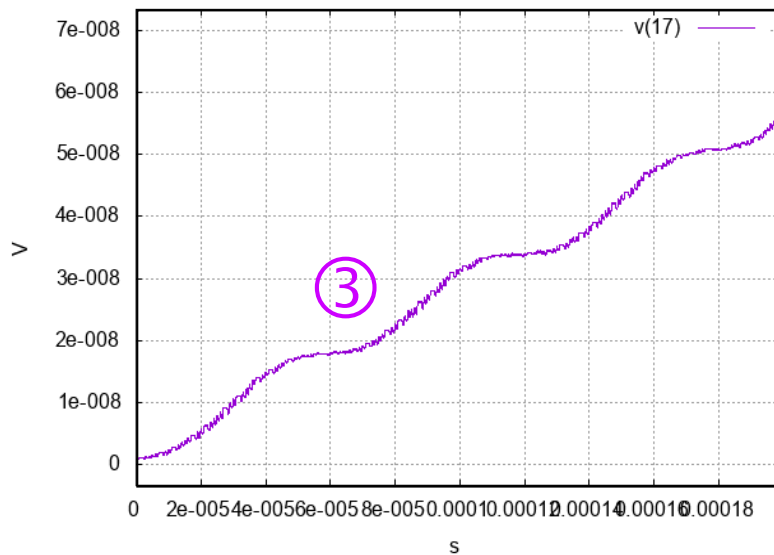

(e) Q2LAL + inverter


Cumulative dissipation

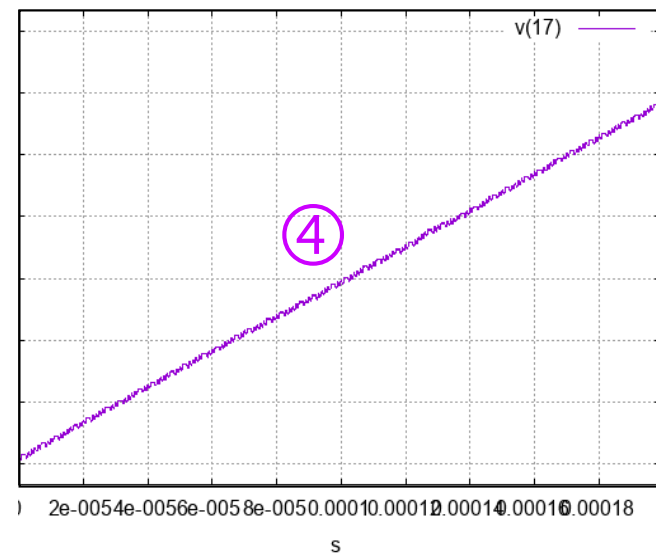


# CMOS vs. CATC noise

- CMOS noise from delta functions with frequencies determined by devices
- CATC Noise from clock
- Below same vertical but 15× expanded horizontal scale

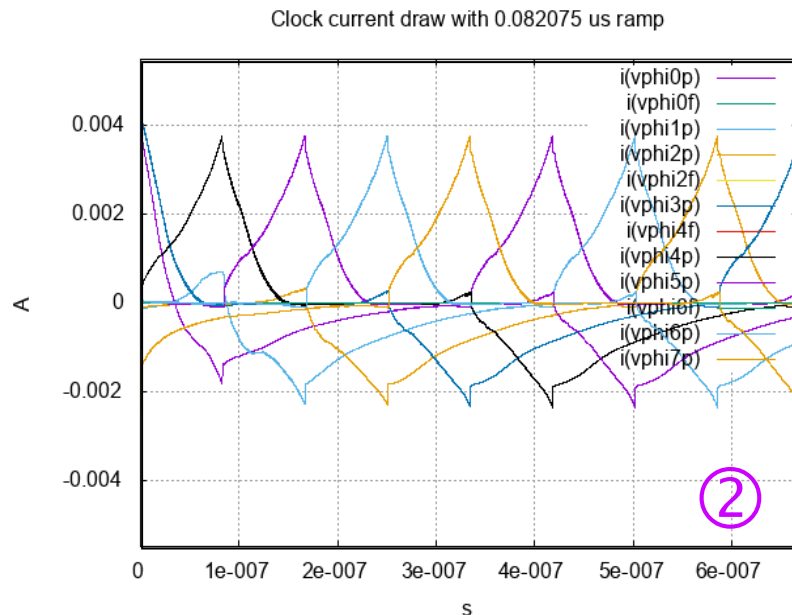
(a) Power-clock current at a reference clock period



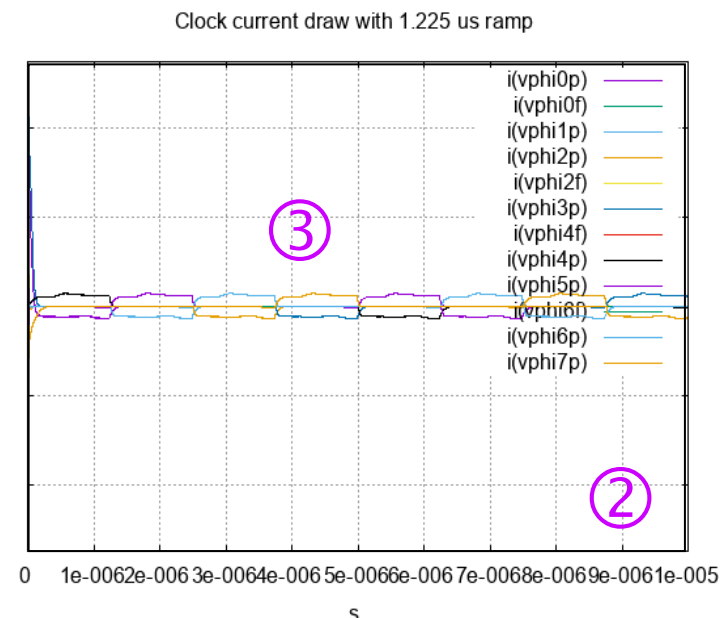(b) Power-clock current at 15× clock period



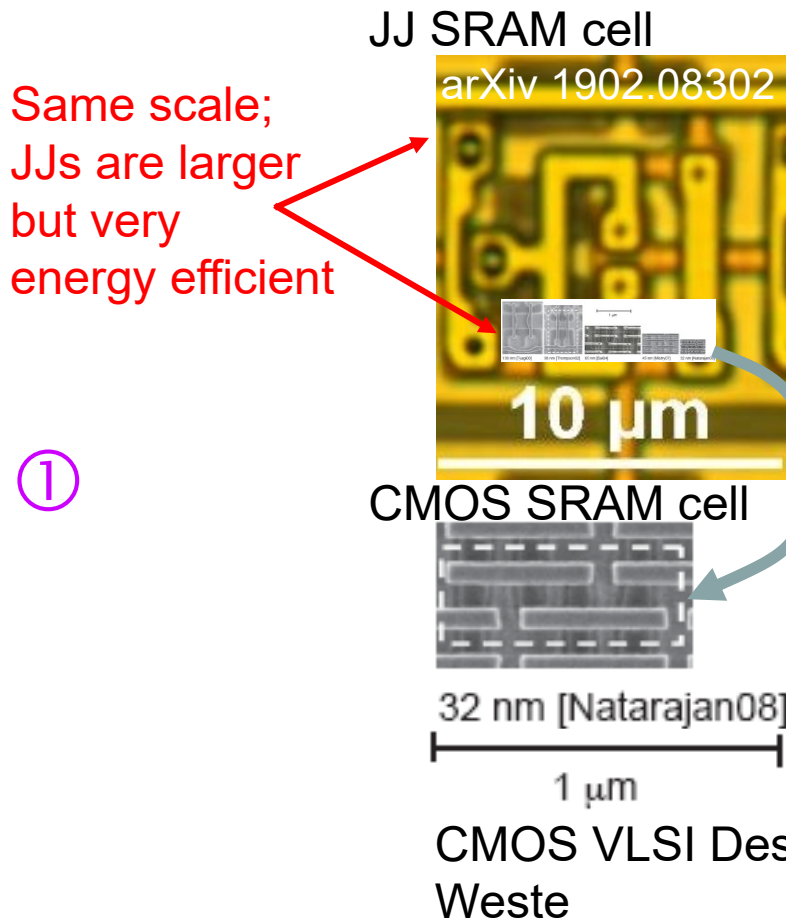
# Single Flux Quantum (SFQ) and CATC Hybrid



- CATC vs. JJ/SFQ
- ② – CATC 1000 $\times$  smaller
  - Same energy
  - CATC 1000 $\times$  slower
- Why would you want JJs plus a lot of slow transistors?
- ③
  - Memory
  - Complex logic


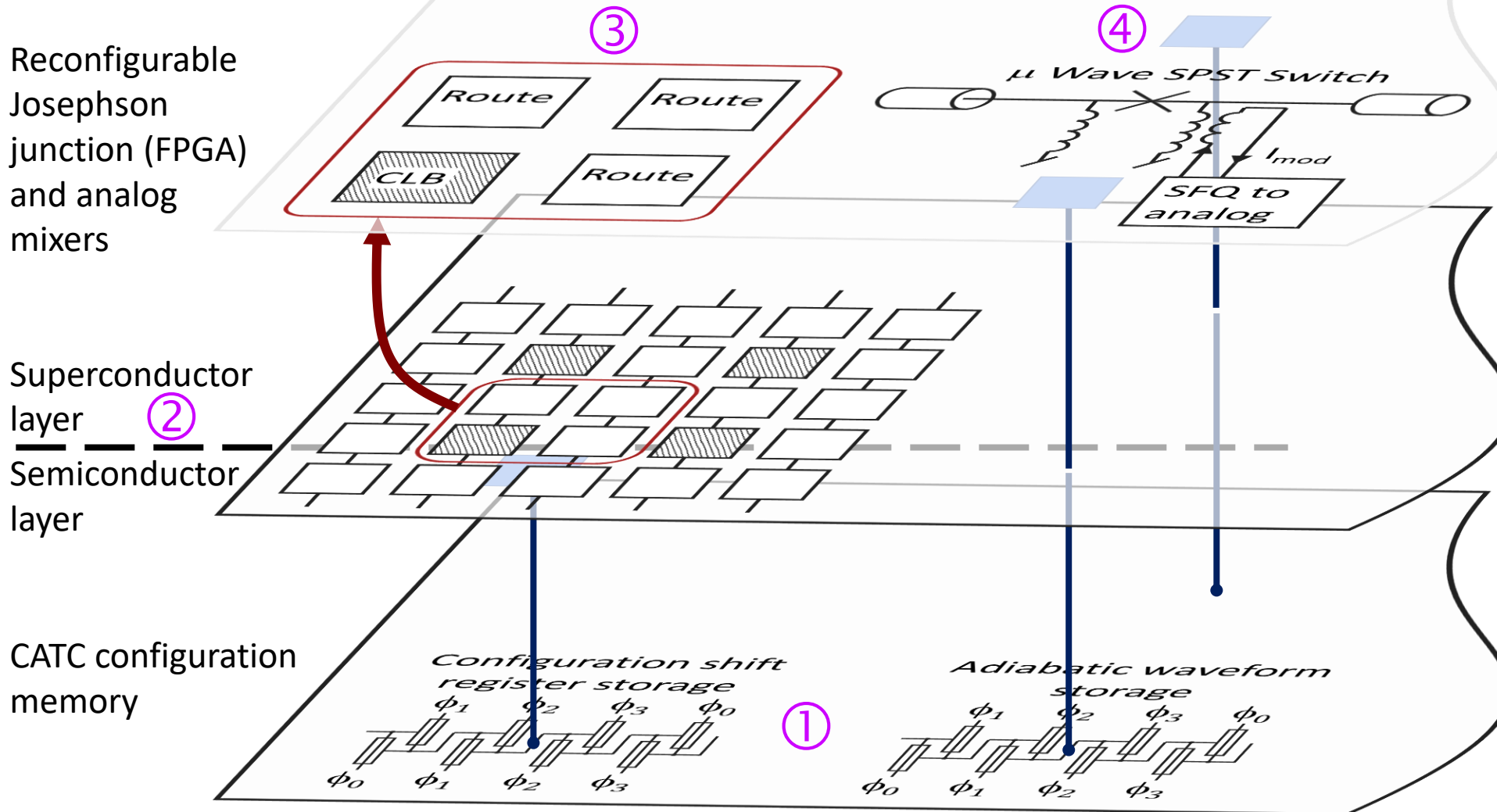
# Transistors/JJ Hybrid Exploits Energy-Delay-Size Tradeoffs



# Conclusions

- Adiabatic circuits not new, but use case is new
  - First part of this talk could have been made 30 years ago
  - But the use case didn't exist, i. e. bypass the cryostat
- Benefits today:
  - 99% - 99.9% heat bypasses the refrigerator, permit scaleup
  - Lower noise in terms of power, noise, and bandwidth
- Future
  - Physical demo in quantum control use case
- For more information see <https://zettaflops.org/q2lal>
  - Preprint of extended abstract; Q2LAL circuit paper